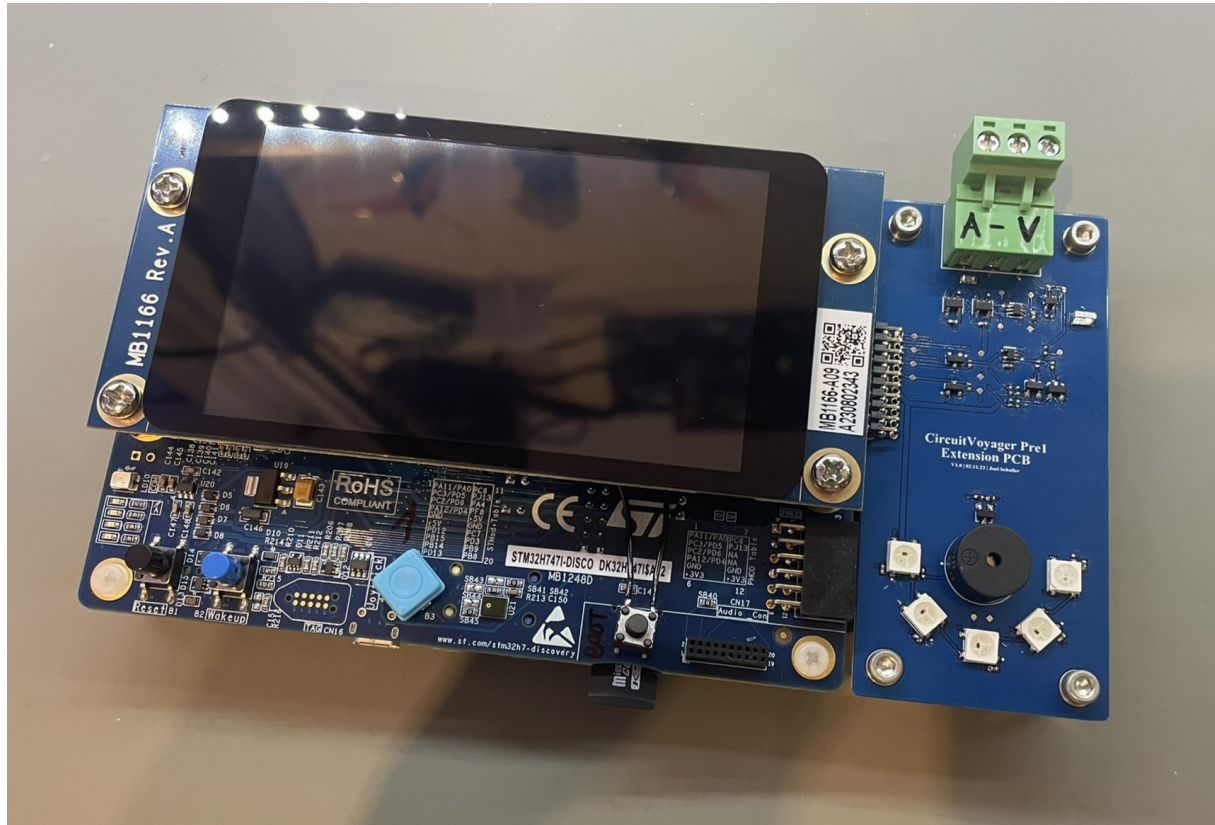


HST Project S5

CircuitVoyager Pre1



Submitted by:
Joel Schaller

Lecturer: Enrico Malacarne

22.09.2023

Abstract

Konzept (gestalterisch)

Methode

Wichtigste Ergebnisse

Contents

| | | |
|----------|---|-----------|
| 1 | Introduction | 1 |
| 1.1 | "Lastenheft" | 1 |
| 1.2 | Mindmap | 2 |
| 2 | Main Body | 3 |
| 2.1 | "Pflichtenheft" | 3 |
| 2.2 | Extension PCB | 4 |
| 2.3 | The MCU | 15 |
| 2.4 | STM32 Multicore Debugging | 15 |
| 2.5 | Boot Problems | 17 |
| 2.6 | QSPI Flash | 18 |
| 3 | Conclusion | 21 |
| 3.1 | Project Start | 21 |
| 3.2 | Time Plan | 21 |
| 3.3 | HW development | 21 |
| 4 | Appendix | 22 |
| 4.1 | Journal | 22 |
| 4.2 | Weekly plans | 24 |
| 4.3 | GANTT Chart | 26 |
| 4.4 | Project Agreement | 27 |
| 4.5 | Interview 1 | 28 |
| 4.6 | Extension PCB Schematics | 29 |
| 4.7 | Extension PCB Manufacture 11.23 BOM | 30 |
| 5 | Credits | 31 |
| | Bibliography | 32 |
| | List of Figures | 33 |
| | List of Tables | 34 |
| | Listings | 35 |
| | Acronyms | 37 |

1 Introduction

The goal of this project is to develop a tiny extension Board for the STM32H747i-Disco Board, to allow it to act as a DMM. Additionally, a SW, that measures the DMM Values and displays them on the Touch Display. If there's more time I could extend the Project with Measurement Logging via a SD-Card or over USB to a Desktop application.

I want to learn how to implement high speed protocols such as Mipi DSI or QPSI. Later in the last year of my apprenticeship I'd like to develop a whole DMM on my own, but with a different approach as standard ones like these from Fluke. For example, I want to make the DMM rechargeable and modernize it a bit.

To realize this project I'm going to use the following tools: Altium Designer, STM32-CubeIDE, LaTeX, TouchGFX.

Also I won't make a diary, because it's easier for me to write my findings down sorted by theme rather than date. But to keep the chronological order of the stuff I've done, there's a Journal in Chapter: [4.1].

1.1 "Lastenheft"

This is a request from the imaginary customer, I'm making this project for:

I need a prototype for a DMM, that can measure voltage, current and continuity. The DMM should have a touchscreen that displays said values. The UI should be intuitive, so everyone who's ever used a DMM can use it to. Normal features as hold, minmax should be available and it would be great if you could fit in a power mode, where the DMM uses the voltage and current measurement to calculate the drawn power from the measured device. Because this project will only be used for the proof of concept, the DMM doesn't have to support mains voltage and we also won't need any safety circuits, AC measuring or negative voltages / currents. It's mainly about the SW. So you can also use DevBoards if there are any available.

1.2 Mindmap

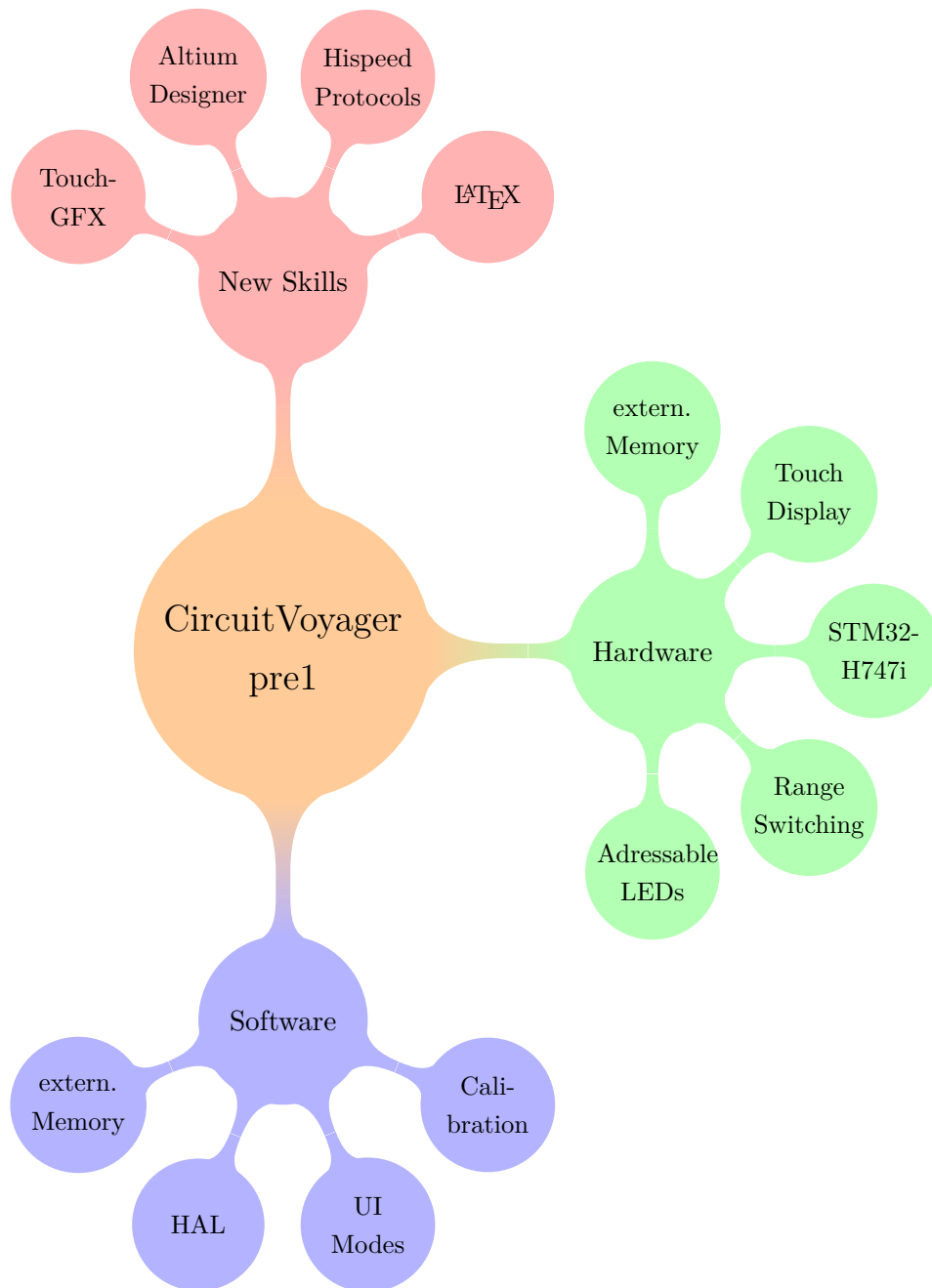


Figure 1.1: Project Mindmap

2 Main Body

2.1 "Pflichtenheft"

Cost

I've already bought two DevBoards one of them stays at TBZ and the other is at home. One of these boards was paid by Mr. Malacarne. Further expenses from the **pcb!** will be paid by me and shouldn't exceed about 50 CHF, as the HW isn't that complicated.

Time

The most time of the project I will work at home because it's a rather big project to execute in one semester. I will also have much time in the fall holidays to work on it. The project will approximately take 100h to complete. Also the more detailed timeplan is in chapter: [4.3]

Tools

To realize this project I will mainly use, the SW STM32CubeIDE with HAL, STM32 CubeProgrammer and Altium Designer. The documentation is written in LaTeX in VSCode. And I'm planning to order the PCB on JLCPCB and I will populate and reflow the PCB at ETHZ, where I'm also allowed to use the measurement equipment for the HW tests.

Technical Details

| value | min. | typ. | max. | unit | description |
|--------------------|------|------|------|------|-------------|
| supply voltage | | 5 | | V | over USB |
| curent to measure | 0 | | 1 | A | |
| voltage to measure | 0 | | 10 | V | |

Table 2.1: Technical Details

2.2 Extension PCB

2.2.1 STMod+

Interface from DevBoard to Extension PCB.

- 5V Supply
- SPI
- I₂C
- ADC
- Interrupt
- PWM
- GPIOs

I will use the STMOD#14 connection that was intended to use as PWM, as a second ADC input. To measure current and voltage at the same time to later show the power consumption of the DUT.

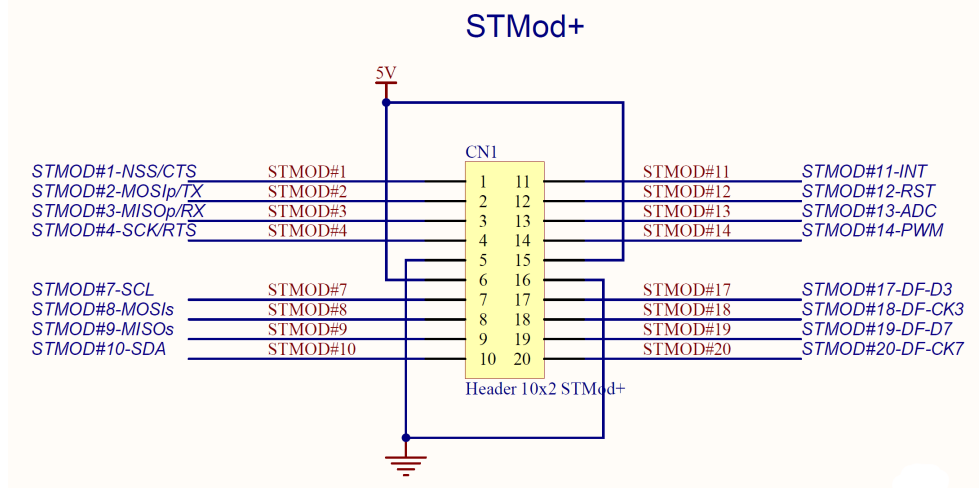


Figure 2.1: STMod+ Interface

2.2.2 Hardware concept

After some thoughts I came up with the following HW concept.

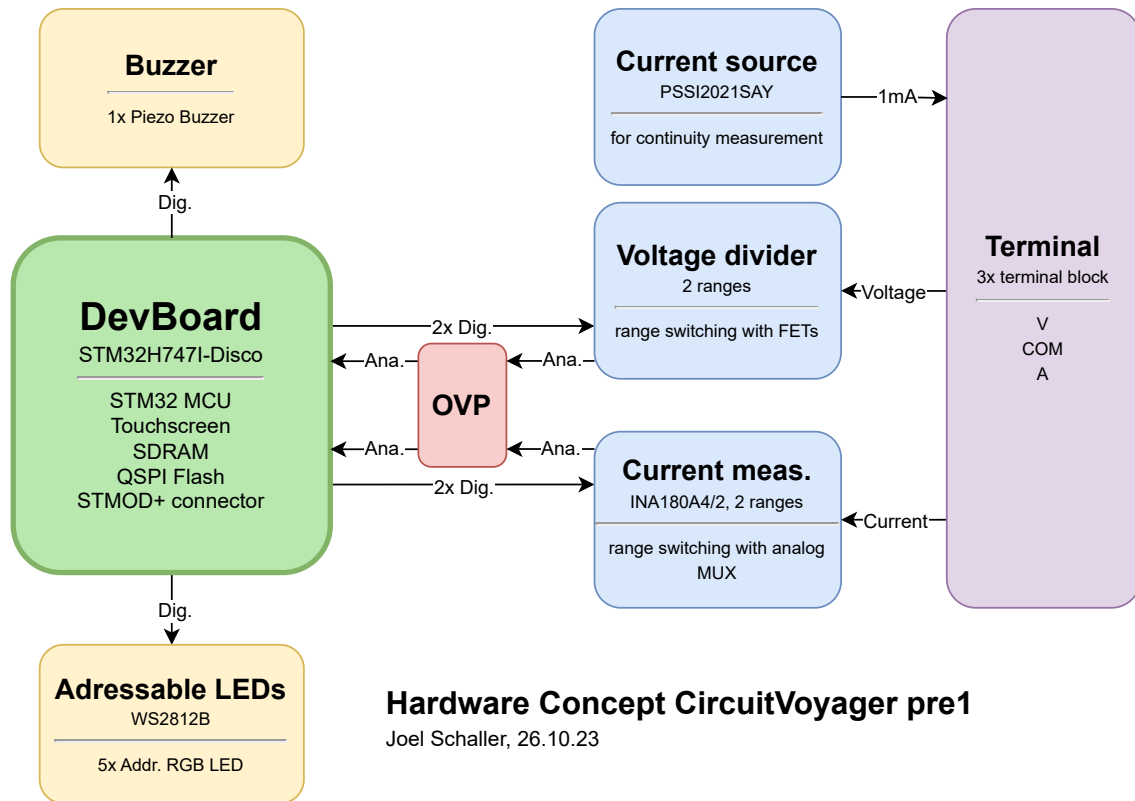


Figure 2.2: Extension PCB HW concept

Voltage measurement

To measure voltage, the DUT should be connected to the terminals V and COM. COM is connected internally to device GND. The V terminal is connected to the Voltage divider block. This block divides the input voltage down, so the ADC in the MCU doesn't overshoot. There are 2 ranges to measure voltage, which can be chosen by setting 2 digital output, that go from the MCU to the voltage divider. There's also an OVP, to protect the MCU from voltages higher than 3.3V. [1]

Current measurement

To measure current, the DUT should be connected to the terminals A and COM. COM is connected internally to device GND. The A terminal is connected to current measurement block. This block measures the current, by letting the current flow through one of two shunt resistors. The DMM can choose which resistor and

therefore range should be selected with the 2 digital Output that are connected from the MCU to the current measurement block. The voltage over the selected shunt is then amplified, by a current amplifier IC and then measured by the MCUs ADC. There's also an OVP, to protect the MCU from voltages higher than 3.3V. [1]

Continuity measurement

To measure continuity, both the voltage divider and the current source is used. The continuity between the V and COM pins is measured. For this a constant current produced by the current source is flowing out of the V terminal. Simultaneously the voltage across those terminals is measured and the resistance / continuity can be evaluated. If continuity is detected, either the buzzer beeps or the LEDs blink. [1]

2.2.3 Schematic

The schematic took me a bit longer than usual, because it's my first whole HW project in Altium before I used KiCAD and Altium is a lot more features and in my opinion is harder to learn. The schematic is in the Appendix 4.6.

Buzzer Circuit

 


Figure 2.3: Buzzer Circuit

This is an active buzzer. If the BUZ line is pulled high by the MCU, the MOSFET starts to conduct and the buzzer starts beeping. This circuit will be used to give an acoustic feedback to the user, if for example a continuity has been detected.

The resistors R3 and R5 build a voltage divider with a ratio of 1/10. This has the advantage, that the gate capacitance of Q1 is charged with a limited current and if nothing's connected to the BUZ net the MOSFET turns the buzzer off and the whole machine isn't in an indeterminate state.

The resistor R2 limit the current flowing through LS1. As LS1 is rated for 30mA at 3V.

$$R_2 = \frac{U_{VCC} - U_{LS1}}{I_{LS1}} = \frac{5V - 3V}{30mA} = \underline{\underline{66.\bar{6}\Omega}}$$

$$P_{R2} = I^2 \cdot R = (30mA)^2 \cdot 66.\bar{6}\Omega = \underline{\underline{60mW}}$$

Finally, I've chosen a 220Ω resistor for R2. With this value the sound should be enough loud, that the user hears it. And the power loss of the resistor will be smaller. That means it should be perfectly fine to use a 0402 resistor that is rated for 62.5mW.

Adressable LEDs Circuit

 


Figure 2.4: Adressable LEDs Circuit

An other option to show if continuity has been detected are these LEDs. The advantage of them is, that they only need one data connection and already include their logic and driving circuits. I've equipped the with one bulk C each, because they're integrated components and they're driven over the 5V rail, which they're specified for. But if they're driven by 5V they theoretically detect all voltages over 3.5V as a logical high. But the MCU only output 3.3V. I've used those LEDs much in past projects and this was never a problem, so I'm assuming that it should also work this time.

Overvoltage Protection Circuit

 


Figure 2.5: Overvoltage Protection Circuit

My Problem is, that the voltages coming from the Extension PCB, can't exceed 4V according to the MCUs datasheet. But because this PCB is powered by the 5V rail, theoretically these voltages could damage the MCU. So the goal was to develop a circuit which protects the ADC inputs. The first idea that came to my mind was to use varistors. I've already used the once in a project, but after reading some application notes on this topic, I decided to use a zenerdiode for the OVP. [2] The zenerdiode I've used has a nominal zenervoltage of 3.6V (max. 3.78V) at 20mA. Together with R13 this should result with a maximum voltage of 3.78V at the ADC inputs. As long as the PREOV voltage doesn't exceed 5.6V.

$$U_{PREOV(MAX.)} = R_{13} \cdot I_Z + U_Z = 100\Omega \cdot 20mA + 3.6V = \underline{\underline{5.6V}}$$

$$P_{R13} = R \cdot I^2 = 100\Omega \cdot (20mA)^2 = \underline{\underline{40mW}}$$

Voltage Divider Circuit

 


Figure 2.6: Voltage Divider Circuit

The voltage divider is used to measure voltages over the V terminal. This circuit is one approach to range switching, which is described more detailed in the following chapter [Write more detailed text about how to execute range switching and what are the pros and cons. Minimum 3 options]. This voltage divider features 2 ranges and I came up with this idea by myself. The ranges are calculated as following:

$$U_{OL(R1)} = \frac{(R_4 + R_7) \cdot U_{OL(MCU)}}{R_7} = \frac{(4.7M\Omega + 10M\Omega) \cdot 3.3V}{10M\Omega} = \underline{4.851V}$$

$$U_{OL(R2)} = \frac{(R_4 + R_8) \cdot U_{OL(MCU)}}{R_8} = \frac{(4.7M\Omega + 2.2M\Omega) \cdot 3.3V}{2.2M\Omega} = \underline{\underline{10.35V}}$$

This divided voltage is then fed into an impedance converter which guarantees that the voltage divider isn't manipulated by the ADC internal resistance and also helps on the DevBoards analog paths, because they're very long and therefore vulnerable to electromagnetic fields.

Text to put into ranges part: This range switching part has the advantage of using many ranges at once, as for example with 2 range switches can use 3 different ranges and with 3 range switches can use 7 ranges. On the other hand it has the disadvantage of only being able to divide

the input voltage and not being able to amplify. Additionally, the internal resistance is always changing and therefore impacting the DUT. I wouldn't recommend this circuit because of said factors and only switch on the measured side. For example use different Amps / Divs to create the right voltage ranges and only switch the high Z path, that doesn't have an impact on the DUT.

Current Source Circuit

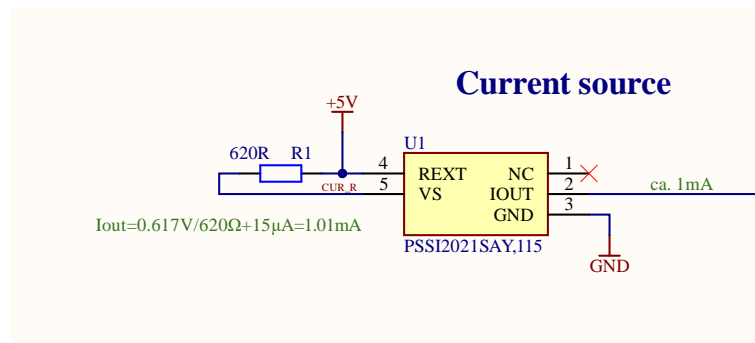


Figure 2.7: Current Source Circuit

The current source circuit will be used to measure continuity and resistance together with the voltage measuring function. A constant current will be induced to the DUT and because the voltage over the DUT can be measured, the resistance can be calculated. The constant current can be calculated as following:

$$I_{OUT} = \frac{U_{VS}}{R_1} + 15\mu A = \frac{0.617V}{620\Omega} + 15\mu A = \underline{\underline{1.01mA}}$$

But this doesn't matter that much, because the DMM will be calibrated using the solderbridge J1.

Current Measuring Circuit

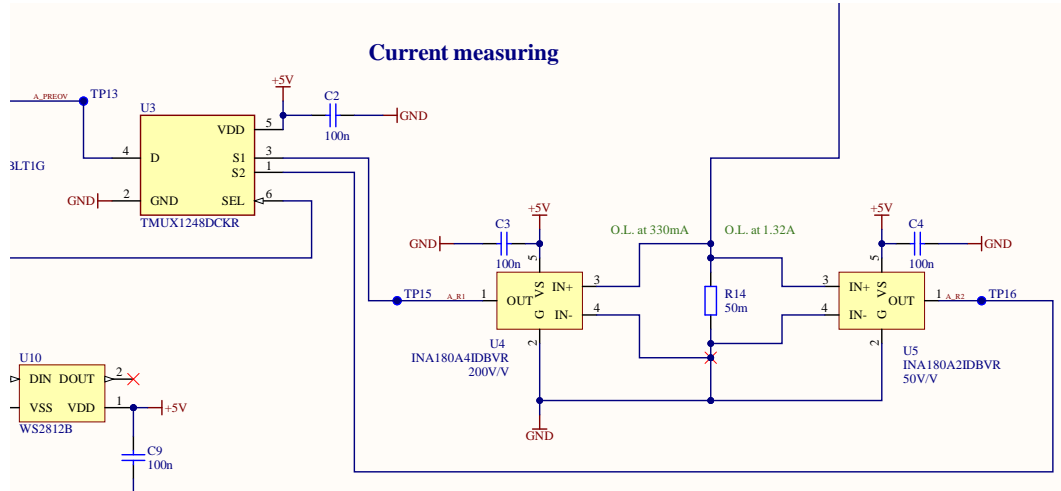


Figure 2.8: Current Measuring Circuit

The current measuring circuit is used to measure currents with the A terminal. This circuit is one approach to range switching, which is described more detailed in the following chapter [Write more detailed text about how to execute range switching and what are the pros and cons. Minimum 3 options]. This circuit features 2 ranges and I came up with this idea, while reading some articles on DMMs [3] [4]. The ranges are calculated as following:

$$I_{OL(R1)} = \frac{U_{OL(MCU)}}{R_{14} \cdot G_{U4}} = \frac{3.3V}{50m\Omega \cdot 200\frac{V}{V}} = \underline{\underline{330mA}}$$

$$I_{OL(R2)} = \frac{U_{OL(MCU)}}{R_{14} \cdot G_{U5}} = \frac{3.3V}{50m\Omega \cdot 50\frac{V}{V}} = \underline{\underline{1.32A}}$$

These voltages are then fed into an analog MUX, which switches the processed voltages to the ADC. This has the advantage, that the DMM doesn't manipulate the actual path, where the current is flowing through and therefore not influencing the DUT.

The power rating of R14 is 125mW, while the maximal power loss of R14 at 1.32A is 87.12mW.

$$P_{R14} = I^2 \cdot R = (1.32A)^2 \cdot 50m\Omega = \underline{\underline{87.12mW}}$$

2.2.4 PCB

Layout

The PCB layout was also made in Altium Designer. This was therefore also my first layout in Altium Designer. The only problem I had, were the vias and improvised them by setting their parameters manually.

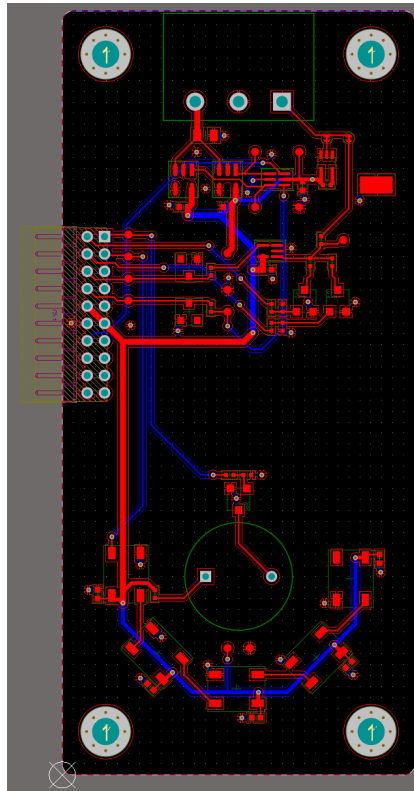


Figure 2.9: Extension PCB Layout

Later I've generated the output files (Gerber files, BOM, assembly drawing) and ordered the PCB on JLCPCB with 2 layers, tented vias, removed order number and blue solder mask. The BOM is in the appendix chapter: 4.7. The components were sourced using DigiKey and ETH SPH.

Assembly

Then I've assembled the PCB by hand, which wasn't a problem at all. But it turned out, that I've ordered the wrong connectors for the STMod interface. Instead of the 4 mm long pins I've ordered the 2 mm long pins, which don't make contact with the socket from the DevBoard. But luckily I was able to order longer ones, which arrived quite fast.

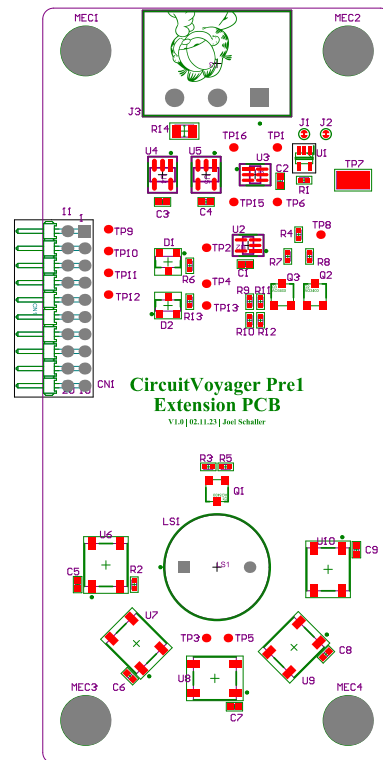


Figure 2.10: Extension PCB Assembly Drawing

 


Figure 2.11: Extension PCB

PCB Bild durch echtes bild ersetzen.

Commissioning

2.3 The MCU

For this project I've chosen a high speed microcontroller. I'm using an STM32H747-XIH6U. The special thing about this MCU is, that it has 2 cores. The main core is a Cortex M7 at a frequency of up to 480MHz and the second one is a Cortex M4 running at up to 240MHz. But this also means that it's a bit expensive at about 20 CHF. This MCU also features 1 MB of flash per core and a total of 1 MB of RAM. But these memories can get full rather quickly, when working with graphical displays or the USB stack for example. That's why I'm using an external flash and RAM in this project.

2.4 STM32 Multicore Debugging

As usual, I'll be testing the DevBoard by programming a good old blink sketch. The information for this multicore blink sketch I got from Controller Tech's YouTube channel [5], because the official SW documentation from STM isn't that good, and therefore I wasn't able to get the information I needed to run my first sketch.

2.4.1 Procedure

1. Create a project with the STM32 Cube template for the STM32H747XIH6. (Using default configuration)
2. Set up the RCC to use the external oscillator and configure clocks to their maximum frequencies.
3. Set up the GPIOs of for the debug LEDs. Special is, that you have to assign a core to each GPIO pin. This parameter says, which core is able to manipulate said GPIO and in which under project (CM4 or CM7) has the define with the GPIO name defined.

| STM32 pin | LED number | LED color | Name in code | Core |
|-----------|------------|-----------|--------------|------|
| PI12 | LED1 | Green | LED_G | CM7 |
| PI13 | LED2 | Orange | LED_O | CM7 |
| PI14 | LED3 | Red | LED_R | CM4 |
| PI15 | LED4 | Blue | LED_B | CM4 |

Table 2.2: LED Annotation

4. Under: Project Manager → Code Generator: Enable the option: "Generate Peripheral initialization as a pair of .c/.h files per peripheral".
This should make the project more structurized.
5. Generate code.
6. Now 2 under projects are created, for each core one. Rather than using the standard files, that are already full of redundant information, I will create my own main files, with the advantage that they're also easily separable between the CM4 and CM7. The files written by me are stored in the folders "Core/Usercode"
7. Write the code to blink the LEDs for each core:

```
1 #include "usermain_CM4.h"
2
3 void usermain_cm4(void)
4 {
5
6     while(1)
7     {
8         HAL_GPIO_TogglePin(LED_B_GPIO_Port , LED_B_Pin);
9         HAL_Delay(500);
10    }
11 }
```

Listing 2.1: Blink Code CM4

8. Now configure the debug configuration for the CM7: Enable "Halt all cores" and under Startup add the CM4 config with the "Debug" Build configuration selected.
9. Now configure the debug configuration for the CM4: set port to 61237, set reset behaviour type to "None" and under Startup → Edit: uncheck the download option.
10. Now to flash the MCU it's important, that all files are saved, because they're not saved automatically as usually in single core projects. Then Click on the "Run" button, with the CM7 configuration selected, the CM4 won't work.
11. To debug the MCU also save all files and then start debugging with the CM7 configuration selected. After the CM7 session started, click again on the debug

button and start the session for the CM4. Now run both threads simultaneously by selecting them both with the "Ctrl" key and then starting them. After those threads started and the clock is configured, they can be manipulated separately.

Additionally, I'd recommend watching the video from Controllers Tech, as it's really informative. [5] For Example Controllers Tech explains how the startup of the cores work and how you can disable cores. There are also more videos from Controllers Tech in this "Multi Core STM32" series.

2.5 Boot Problems

While programming the MCU for the first times, I had the problem that the MCU wasn't detected sometimes by the ST-Link. Therefore, the MCU wasn't resetable nor new firmware could be uploaded. It turned out, that the ST-Link could program the MCU again, when accessing the BOOT mode, which is intended to boot the MCU over USB DFU. But this mode also stops the MCU from starting the script and therefore the ST-Link detects the MCU. The boot mode can be accessed by shorting the pads of R192. Then the MCUs memory can be erased and after removing the solderbridge, the MCU operates again as normal. After this problem, with the not detectable MCU occurred multiple times, I decided to add a button to access the boot mode. So I don't have to have a soldering iron around, when the MCU ain't detectable. This modification looks as following:



Later it turned out, that those problems came from a faulty RCC configuration. That's something I should investigate further. Because right now I'm only able to get up to 400MHz for the CM7. This probably has something to do with the SMPS and Voltage scaling option in the RCC tab.

2.6 QSPI Flash

To extend the internal flash of the MCU, there is 128MB of QSPI Flash on the DevBoard. In this section I'll try to implement this flash, so I'm able to store the actual firmware on this external flash. This also means, that the MCU should then boot from the external memory.

2.6.1 Write Test

In this first test I'll try to simply write some data to the Flash and therefore confirm, that the communication between the MCU and flash works as intended. For this I've again followed the instructions from Controllers Tech on YouTube. [6]

1. Enable QSPI block in "Dual Bank with Quad Lines" mode (Because DevBoard uses two ICs, each 512Mbit) for CM7.
2. Set up pins according to the schematics. (standard cube config is wrong.)
Configure Pins to CM7 in "very high" speed mode.
3. Enable chip select 1 for both banks.
4. Set clock prescaler to 2. (200MHz Clock divided by 2 to the power of 2 → 50MHz) (Flashs max. frequency in DTR mode (dual bank) is 90MHz)
5. Fifo threshold to 4.
6. Sample shifting to "Sample Shifting Half Cycle"
7. Flash size to 26. (Flash size is 2 to the power of 26 + 1 Bytes. → 128MB)
8. Chip select high time to "6 Cycles"
9. For Cortex-M7 Enable: ICache and DCache.
10. Generate code.
11. Then add user code lines from STM GitHub. [7] to qspi.c and qspi.h.

Now you can download the firmware to the MCU. And verify, that no error is triggered. (Orange LED blinking) Then to verify, that the string was written to the flash: open STM32CubeProgrammer and enable the external loader for the H747-Disco DevBoard. Now at the address 0x90000000, the string "msgOut" should be shown.

```
1 #include "usermain_CM7.h"
2
3 uint8_t* msgOut = (uint8_t*)"1234567890";
4
5 void usermain_cm7(void)
6 {
7     if(CSP_QUADSPI_Init() != HAL_OK)
8     {
9         Error_Handler();
10    }
11
12    if(CSP_QSPI_Erase_Chip() != HAL_OK)
13    {
14        Error_Handler();
15    }
16
17    if(CSP_QSPI_WriteMemory((uint8_t*)msgOut, 0, strlen((char
18    *)msgOut)) != HAL_OK)
19    {
20        Error_Handler();
21    }
22
23    while(1)
24    {
25        HAL_GPIO_TogglePin(LED_0_GPIO_Port, LED_0_Pin);
26        HAL_Delay(500);
27    }
```

Listing 2.2: QSPI Write Test CM7

While playing a bit with this code, I've noticed, that the flash can't manipulate single bits. It can just turn a 1 into a 0 but not in reverse. To set a 0 to a 1 you have to erase a whole sector or the whole chip. After some research on this topic I've learned, that this behaviour is common for flash memories, as they're normally

only used to store data over a long time. For example: Firmware.

2.6.2 Boot from QSPI

After trying to boot from the QSPI flash, I decided to change my plans and go on without a bootloader and external RAM. At the moment I don't know to less debug the problems I've had and therefore I decided to go on with the easier tasks of this project like the actual measurements and move the Memories implementation to another project.

3 Conclusion

3.1 Project Start

I've noticed that it was quite hard for me to start with the project. There are so much topics to imply, that it can get overwhelming and very emotional. I've also underestimated the time needed to set up the documentation LaTeX files and the whole planning. It can be demotivating if you're spending a lot of time and in the end didn't really start with the project. But later I was able to start the project without much trouble.

3.2 Time Plan

3.3 HW development

I've learned much in this project part. Mainly this was Altium Designer, as this was my first complete project I've realised in Altium Designer. This also led to some not nicely solved solution. All components for example have their own properties and this leads to a unreadable BOM.

But in the end I've also noticed, that the dataflow (that usually should go from left to right) goes in the wrong direction. This had already started in the HW-Chart and therefore also ended up in the schematic.

I've also used Draw.io one of the first times and by now it looks very promising. It's much easier and more straight forward than MS Visio. Everything just works as intended.

Gesamtschau, Arbeitsergebnis, Gesamturteil, evtl. Ausblick, was ich lernen konnte

4 Appendix

4.1 Journal

| Date | Location | Duration | Activity |
|------------|----------|----------|--|
| 01.09.2023 | TBZ | 1.5h | Selected and bought DevBoard |
| 08.09.2023 | TBZ | 2h | Tested DevBoard with demos |
| 08.09.2023 | TBZ | 0.5h | Noted first ideas for DMM |
| 15.09.2023 | TBZ | 1.5h | Written and signed Project Agreement [4.4] |
| 21.09.2023 | Home | 3h | Created documentation template |
| 22.09.2023 | TBZ | 2h | Started writing Journal [4.1] |
| 24.09.2023 | Home | 1.5h | Made GANTT chart [4.3] |
| 27.09.2023 | Home | 2h | Written detailed planning and introduction |
| 29.09.2023 | TBZ | 1.5h | Added mindmap, Lasten-, Pflichtenheft |
| 06.10.2023 | TBZ | 1h | Started with block diagram (extension PCB) |
| 20.10.2023 | ETH | 0.5h | Started Altium Project, Schematic template |
| 23.10.2023 | ETH | 3h | HW Concept / documentation |
| 23.10.2023 | ETH | 3h | Start schematic / documentation |
| 25.10.2023 | Home | 2h | Schematic: Current Src, Volt div |
| 26.10.2023 | ETH | 1.5h | Schematic: Current meas, ERC |
| 26.10.2023 | Home | 1h | Schematic: Cleanup, Comments, DS Saves |
| 26.10.2023 | Home | 1h | Documentation & prepared Interview 1 |
| 27.10.2023 | TBZ | 1.5h | Documentation: Started with schematic part |
| 28.10.2023 | Home | 2h | Documentation: schematic parts |
| 29.10.2023 | Home | 1h | Docu: schematic done, resources cleanup |
| 29.10.2023 | Home | 0.5h | Layout: Outline, Placement start |
| 31.10.2023 | Home | 1h | Layout: Placement Done |
| 01.11.2023 | Home | 1.5h | Layout: Routing Done |
| 02.11.2023 | Home | 1h | Layout: Cleanup & Export |
| 03.11.2023 | TBZ | - | Interview 1: signed by mala |
| 03.11.2023 | TBZ | 1h | Pepered BOM for supplying |
| 04.11.2023 | Home | 1h | Documentation: PCB, Reflection |

Table 4.1: Project Journal 1

| Date | Location | Duration | Activity |
|------------|----------|----------|--------------------------------------|
| 05.11.2023 | Home | 0.5h | STM32 Multicore Debugging |
| 05.11.2023 | Home | 1h | Documentation: STM32 Multicore Debug |
| 05.11.2023 | Home | 1h | Boot problems / HW MOD |
| 09.11.2023 | Home | 3h | Population of 2 Extension PCBs |
| 11.11.2023 | Home | 0.5h | HW MOD of second DevBoard |
| 14.11.2023 | Home | 2h | QSPI Write test and documentation |
| 23.11.2023 | Home | 3.5h | QSPI: tried to Ext. boot |

Table 4.2: Project Journal 2

4.2 Weekly plans

4.2.1 KW39 & 40

- Write introduction
- Planning: Cost, Tools, When, Why
- Create project diagram (learning process)
- "Lastenheft"
- "Pflichtenheft"
- Make a HW-Digram for the Extension **pcb!**.
- Make the schematic of the Extension **pcb!**.
 - Part to measure voltage.
 - Part to measure current.
 - Part to measure continuity.
 - Addressable LEDs.
- Start with the Layout of the Extension **pcb!**.
- Reflection of the start of the project.

4.2.2 KW41 & 42

Fall holidays. I planned to invest much time in the holidays, but it turned out that my plans changed, and I was busy.

4.2.3 KW43 & 44

Mainly catching up.

- Make a HW-Digram for the Extension **pcb!**.
- Make the schematic of the Extension **pcb!**.
 - Part to measure voltage.
 - Part to measure current.
 - Part to measure continuity.

- Addressable LEDs.
- Make the whole Layout of the Extension **pcb!**.
- Order the Extension PCB and the components.
- Reflection of the start of the project.

and maybe if the time is sufficient I could start with implementing the SDRAM and QSPI Flash.

4.2.4 KW45 & 46

- Populate and commission the extension PCB.
- Implement QSPI flash with bootloader.
- Implement external SDRAM.
- Implement touch display. (MIPI DSI, Touch)

and maybe if the time is sufficient I could start with learning TouchGFX.

4.3 GANTT Chart

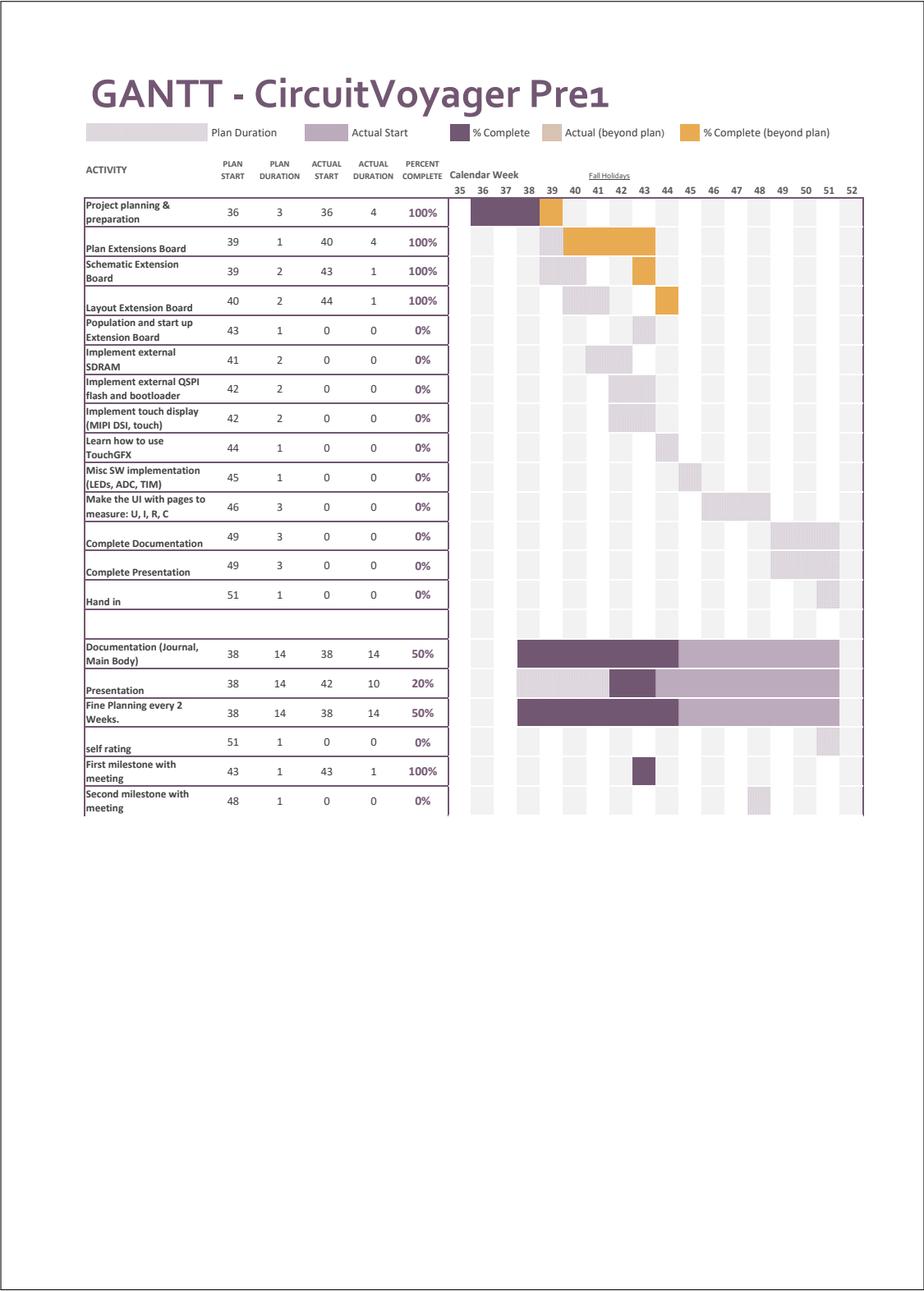


Figure 4.1: GANTT Chart

4.4 Project Agreement

| | | |
|-------------------------|---|-------------------------------------|
| Information HST: BÜP | TBZ/EE / 2337.00 jschaller Sem: 5 | HST 1_Project_Agreement.docx |
|-------------------------|---|-------------------------------------|

TBZ
 Technische Berufsschule Zürich
 Abteilung Elektro/Elektronik

1 Projektvereinbarung

Verfasser/innen: Joel Schaller
Klasse: BEN21
Titel: CircuitVoyager pre1

| | |
|--|---|
| 1. | Thema (Hintergrund, Überblick, gegenwärtiger Wissensstand) Develop a tiny extension Board for the STM32H747i-Disco Board, to allow it to act as a DMM. Additionally, a software, that measures the DMM Values and displays them on the Touch Display. If there's more time I could extend the Project with Measurement Logging via a SD-Card or over USB to a Desktop application. |
| 2. | Eigene Fragestellung / Untersuchungsgegenstand 2.1 Eigene Fragestellung (Leitfrage) How to implement the following functions / protocols? (QSPI Flash, SDRAM, TouchGFX, Mipi DSI) and if the time is sufficient: (FAT with SDcards, Bootloaders) 2.2 Hypothese (Vermutung über das Ergebnis) I want to learn, working with High Speed MCUs and implement such protocols. 2.3 Methoden und Vorgehen (mindestens 2 Methoden müssen angewendet werden) HW-Dev (Altium), SW-Dev (STM32Cube with HAL), Documentation in LaTeX 2.4 Hilfsmittel Internet, literature 2.5 Kontaktpersonen, Informationsstellen, Institutionen Teachers, Instructor at ETH, Dad |
| 3. | Persönlicher Bezug / Motivation In the next 2 Years I want to develop my own DMM, because I think there's much to improve with standard DMMs as Fluke. For Example: Touch Display, Rechargeable Battery... |
| 4. | Bewertungsform This Project will only be done by me. Time: about 28 lesson and unknown time at home. Project delivery on: 12.01.2023 |
| 5. | Besprechungstermine mit Lehrperson (vorgeschrieben sind zwei Besprechungen) Termin 1: 27.10.2023 Termin 2: 01.12.2023 |
| Datum: 15.09.23 Die Lernenden: Datum: 15.9.23 Die Lehrperson: | |
| <small>DMM = Digital Multimeter TouchGFX = Graphical Designer for Embedded Touch Displays</small> | |

BEN21
Seite 1 (1)
1_Project_Agreement.docx

Figure 4.2: Project Agreement

4.5 Interview 1


 

| | | |
|--|--|---|
| Projektbewertung HST / BÜP: Projektarbeit 2023 | MAL / 2109.00 -- Sem: 5 | HST / BÜP 96_Interview_1.docx |
|  TBZ Technische Berufsschule Zürich Abteilung Elektro/Elektronik | | |
| <h3>Protokoll der Zwischenbesprechung</h3> | | |
| Zwischenbesprechung 1 | | Datum: 27.10.23 |
| Name: Joel Schaller | | Klasse: BEN21a |
| Titel der Arbeit: CircuitVoyager pre1 | | |
| Dieses Formular ist soweit möglich ausgefüllt an die Zwischenbesprechung mitzubringen. Weiter sind möglichst alle Unterlagen mitzubringen, vor allem das Geschriebene (Arbeit, Dokumentation, aktuelles Projektjournal, Zeitplan, Notizen, Korrespondenzen) sowie die wichtigsten Informationsmaterialien (Bücher, Datenblätter etc.) | | |
| Stand der Arbeit / Zeitplan | | |
| <ul style="list-style-type: none"> - Viel Doku geschrieben (17 Seiten) mit ganzem LaTeX aufgesetzt. (sehr zeitaufwändig gewesen) - Projektplanung inklusive GANTT, Lasten-/Pflichtenheft. - DevBoard ausgetestet mit Demo Code. - HW Block Diagramm / Konzept erstellt. - Schema aufgesetzt und fertiggezeichnet. | | |
| Nächste Schritte | | |
| <ul style="list-style-type: none"> - Layout für Extension PCB erstellen. - Extension PCB bestücken. - SDRAM und QSPI implementieren. | | |
| Änderung der Projektvereinbarung (Bestätigung und vorliegend Begründung) | | |
| Keine Änderungen, auch wenn ich in meinem Zeitplan sehr hintendrin bin. Doch ich denke ich kann besonders in der Software gut wieder aufholen und werde Alles geben, wieder „on time“ zu sein. | | |
| Probleme, Schwierigkeiten fachlicher Art | | |
| eingetretene und noch zu erwartende Probleme, Massnahmen, Lösungen | | |
| Direkte Probleme hatte ich bisher nicht. Ich kam immer gut an die Infos, die ich brauchte. Jedoch bin ich im Zeitplan etwas hintendrin, wie oben beschrieben. | | |
| Zürich, 03.11.23 | Unterschrift Lehrperson  | |
| Zürich, 27.10.23 | Unterschrift Lernende  | |
| 96_Interview_1.docx | 1(1) | 03.11.2023 / jschaller |

Figure 4.3: Interview 1

4.6 Extension PCB Schematics

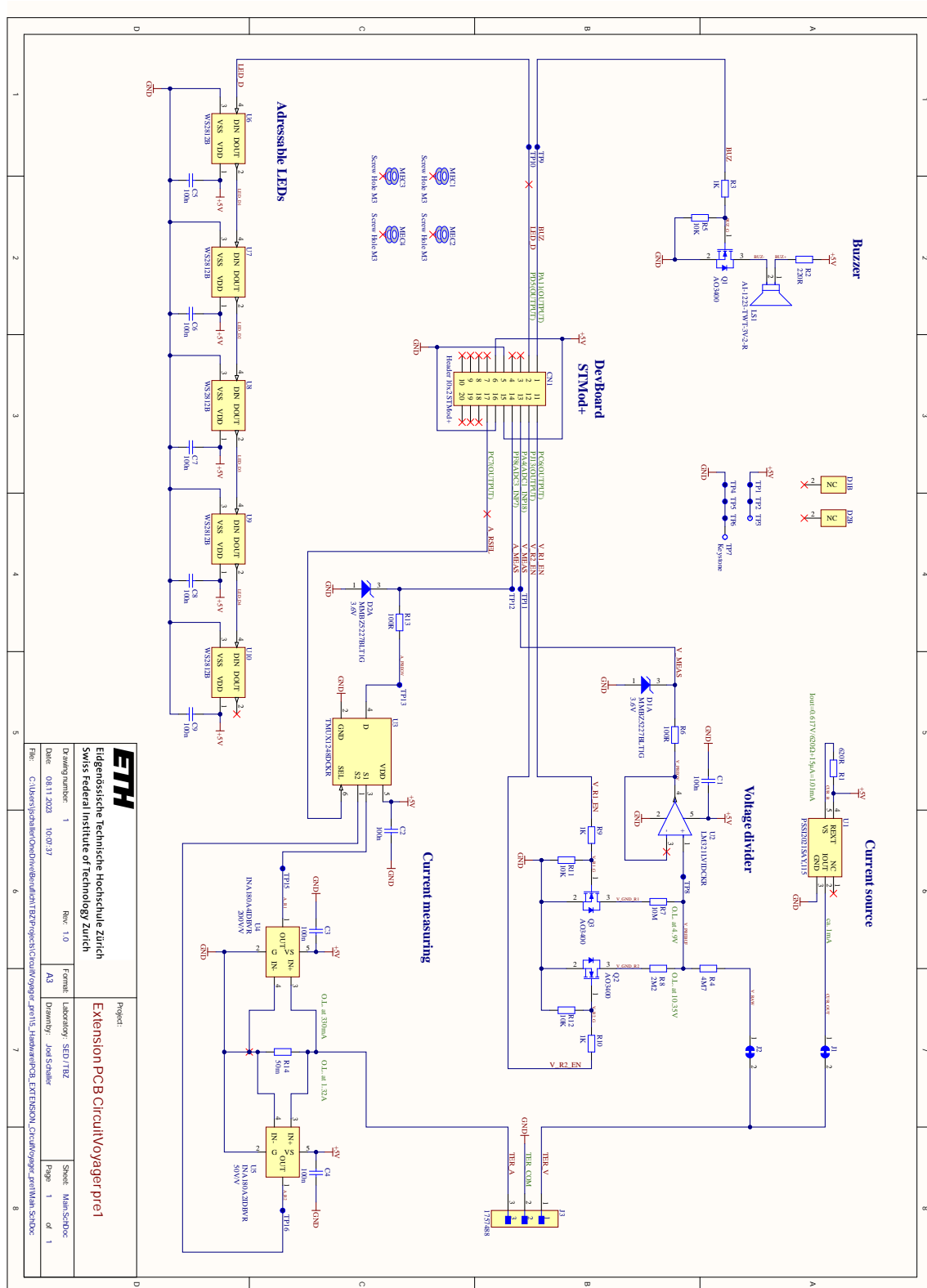


Figure 4.4: Extension PCB Schematics

4.7 Extension PCB Manufacture 11.23 BOM

| Designator | Comment | Value | Description | Quantity | Digi-Key Part number |
|------------------------------------|---------------------|-------------|---|----------|--|
| C1, C2, C3, C4, C5, C6, C7, C8, C9 | C0402 | 100n | CERCAP 100n 16v 5% X7R 0402 | 9 | 311-1338-1-ND |
| CN1 | Header 10x2 STMMod+ | Header 10x2 | Header 10x2, 2mm, RA, TH, Height 3.20mm/3. | 1 | 2073-BF060-20A-B-0200-0280-0305-L-D-ND |
| D1, D2 | MMBZ5227BLT1G | | Zener Voltage Regulator, 225 mW, 3-pin SOT-2 | 2 | MMBZ5227BLT1GOSCT-ND |
| I3 | 1757488 | | TERMI BLOCK HDR 3POS 90DEG SMM | 1 | |
| LS1 | AI-1223-TWTF-3V-2-R | | BUZZER MAGNETIC 3V 12MM TH | 1 | 668-1456-ND |
| Q1, Q2, Q3 | AO3400 | | N-channel Enhancement Mode Field-Effect Tr | 3 | |
| R1 | R0402 | 620R | RES 620R 62.5mW 1% 0402 | 1 | 311-620LRCT-ND |
| R2 | R0402 | 220R | RES 220R 62.5mW 1% 0402 | 1 | 311-220LRCT-ND |
| R3, R9, R10 | R0402 | 1K | RES 1K 62.5mW 1% 0402 | 3 | 311-1.00KLRCT-ND |
| R4 | R0402 | 4M7 | RES 4M7 62.5mW 1% 0402 | 1 | 13-RC0402FR-074M7LCT-ND |
| R5, R11, R12 | R0402 | 10K | RES 10K 62.5mW 1% 0402 | 3 | 311-10.0KLRCT-ND |
| R6, R13 | R0402 | 100R | RES 100R 62.5mW 1% 0402 | 2 | 311-100LRCT-ND |
| R7 | R0402 | 10M | RES 10M 62.5mW 1% 0402 | 1 | 311-10.0MLRCT-ND |
| R8 | R0402 | 2M2 | RES 2M2 62.5mW 1% 0402 | 1 | 13-RC0402FR-072M2LCT-ND |
| R14 | R0805 | 50m | RES 0R05 125mW 1% 0805 | 1 | 13-PE0805FR-F070R05LCT-ND |
| U1 | PSS12021SAV,115 | | NEXPERIA - PSS12021SAV,115 -IC, CURRENT SC | 1 | 1727-4328-1-ND |
| U2 | LM321LVIDCKR | | IC OPAMP GP 1 CIRCUIT SC70-5 | 1 | 296-53426-1-ND |
| U3 | TMUX1248DCKR | | 3-LOW RON, 5-V, 2:1 (SPDT) GENE | 1 | 296-TMUX1248DCKRCT-ND |
| U4 | INA180A4IDBVR | 200V/V | Operational Amplifier, 1 Func, 500uV Offset-M | 1 | 296-47655-1-ND |
| U5 | INA180A2IDBVR | 50V/V | Operational Amplifier, 1 Func, 500uV Offset-M | 1 | 296-47653-1-ND |
| U6, U7, U8, U9, U10 | WS2812B | | Intelligent Control LED Integrated Light Source | 5 | |
| TP7 | KeyStone | | TP SMD 3.81x 2.03mm | 1 | 36-5019CT-ND |
| Digi-Key | | | | | |
| Already supplied | | | | | |

Figure 4.5: Extension PCB Manufacture 11.23 BOM

5 Credits

Bibliography

- [1] ElectroNoobs, “Arduino 5 in 1 multimeter v2.0.” Available at http://electronoobs.com/eng_arduino_tut112.php (2019/11/29).
- [2] A. Walsh, “Protecting adc inputs.” Available at <https://www.analog.com/en/technical-articles/protecting-adc-inputs.html>.
- [3] A. Garaipoom, “Digital multimeter circuit using icl7107.” Available at <https://www.eleccircuit.com/digital-multimeter-circuit-using-icl7107/> (2022/08/16).
- [4] TexasInstruments, “An-202 a digital multimeter using the add3501.” Available at https://www.ti.com/lit/an/snoa592c/snoa592c.pdf?ts=1698230599203&ref_url=https%253A%252F%252Fwww.ti.com%252Fsitesearch%252Fde-de%252Fdocs%252Funiversalsearch.tsp%253FlangPref%253Dde-DE%2526searchTerm%253Dmultimeter%2526nr%253D5689 (2015/02).
- [5] ControllersTech, “Stm32 dual core. getting started with stm32 dual core cpus.” Available at https://www.youtube.com/watch?v=jI1k6p-fduE&list=PL6W_Zc90pVoEW7mhV1fjzXFTc9skCltyI&index=1 (2021).
- [6] ControllersTech, “Qspi in stm32, write and read, n25q.” Available at https://www.youtube.com/watch?v=xIfh_uYy-0U (2021).
- [7] STMicroelectronics, “Github: Qspi flash drivers for stm32.” Available at https://github.com/STMicroelectronics/stm32-external-loader/tree/contrib/QSPI_Drivers/MT25QL512 (2020/11/03).

List of Figures

| | | |
|------|---|----|
| 1.1 | Project Mindmap | 2 |
| 2.1 | STMod+ Interface | 4 |
| 2.2 | Extension PCB HW concept | 5 |
| 2.3 | Buzzer Circuit | 6 |
| 2.4 | Adressable LEDs Circuit | 7 |
| 2.5 | Overvoltage Protection Circuit | 8 |
| 2.6 | Voltage Divider Circuit | 9 |
| 2.7 | Current Source Circuit | 10 |
| 2.8 | Current Measuring Circuit | 11 |
| 2.9 | Extension PCB Layout | 12 |
| 2.10 | Extension PCB Assembly Drawing | 13 |
| 2.11 | Extension PCB | 13 |
| 2.12 | Hardware Boot Button Mod | 17 |
| 4.1 | GANTT Chart | 26 |
| 4.2 | Project Agreement | 27 |
| 4.3 | Interview 1 | 28 |
| 4.4 | Extension PCB Schematics | 29 |
| 4.5 | Extension PCB Manufacture 11.23 BOM | 30 |

List of Tables

| | | |
|-----|-----------------------------|----|
| 2.1 | Technical Details | 3 |
| 2.2 | LED Annotation | 15 |
| 4.1 | Project Journal 1 | 22 |
| 4.2 | Project Journal 2 | 23 |

Listings

2.1 Blink Code CM4 16

2.2 QSPI Write Test CM7 19

Acronyms

CircuitVoyager The Name of the DMM I'm developing.

DevBoard main microcontroller development board. (STM32H747I-Disco)

DMM digital multimeter

HW Hardware

SW Software

SPI Serial Peripheral Interface (low level protocol)

SDRAM Synchronous Dynamic Random Access Memory (external RAM)

UI User Interface

Mipi DSI Digital Serial Interface (Display Protocol)

FAT File Allocation System (Low Level Filesystem)

HAL Hardware Abstraction Layer (STM32 Abstraction Library)

ETHZ Eidgenössische Technische Hochschule

TBZ Technische Berufsschule Zürich

ADC Analog Digital Converter (STM32 unit)

TIM Timer (STM32 unit)

DUT Device under test

OVP Over voltage protection

TouchGFX Graphical UI designer for STM32 **mcu**'s

QPSI Quad SPI

OL Overload

RCC Reset and Clock Control (STM32 unit)

CM4 Cortex M4 (CPU)

CM7 Cortex M7 (CPU)

XIP Execute In Place

MSP Main Stack Pointer