



ARDUINO 5 IN 1 MULTIMETER V2.0

Help me by sharing this post

Share 172

[⏮️PREVIOUS TUTORIAL \(eng_arduino_tut111.php\)](#)

[NEXT PART⏭️ \(eng_arduino_tut112_2.php\)](#)

Months back I've made an Arduino based multimeter that was able to measure quite well voltage, current, capacitance, inductance and resistance. That was soldered on a homemade PCB and with wire connections, you can see that tutorial here ([eng_arduino_tut84.php](#)). But that version had some errors. First of all the circuit was a mess because I wasn't using a professional made PCB and we had a lot of wires. Then, I've used the wrong current sensor so that mode was not working. Also, the worst thing was that we had different inputs for each mode. Usually, multimeters have just only one input for the probes and then a rotary switch to change between modes. That's exactly what I've made in this second version and also a few more improvements. Now we have auto scale mode for all the measurements, we can also measure negative voltage because we use the ADS1115 ADC sensor in differential mode, we can also measure AC voltage because the circuit has a full bridge rectifier and a few more improvements...

Arduino Multimeter V2.0 | All in one: V R C L I



Download the Manual

Start download: Get instant access to expert repairs.

eManualOnline


[

PART 1 - What we need

This project is easy and the part list is quite straightforward. The Arduino will control everything. To detect the angle of rotation and by that know when the ball is upside down we will use the MPU6050 gyro module. To print the text we need an OLED display and to play sounds we will use the DFplayer with the SD card and a small speaker. We need a 18650 battery and a charging module and to get 5V we need a small boost converter. We will also need glue and small wires.


We need:

1 x 3D files case: 3D STL files (eng_arduino_tut112_stl1.php)
1 x PCB: GERBERs files (eng_arduino_tut112_gerber1.php)
1 x ATmega328p AU chip: LINK eBay (https://www.ebay.com/itm/1PCS-MCU-IC-ATMEL-TQFP-32-ATMEGA328P-AU-MEGA328P-AU-ATMEGA328P-MEGA328P/362255972024?hash=item54582376b8:g:BvwAAOSw03lY5gup&mkcid=1&mkrid=711-53200-19255-0&siteid=0&customid=link&campid=5338106513&toolid=20001&mkevt=1)
1 x i2c OLED display: LINK eBay (https://www.ebay.com/itm/1-3-inch-Blue-OLED-LCD-4Pin-Display-Module-IIC-I2C-128x64-3-5V-Interface-f-J1H7/123417873530?epid=19020266461&hash=item1cbc474c7a:g:v3wAAOSwMxJbvjIL&mkcid=1&mkrid=711-53200-19255-0&siteid=0&customid=link&campid=5338106513&toolid=20001&mkevt=1)
.
.
See full part list... (eng_arduino_tut112_parts1.php)

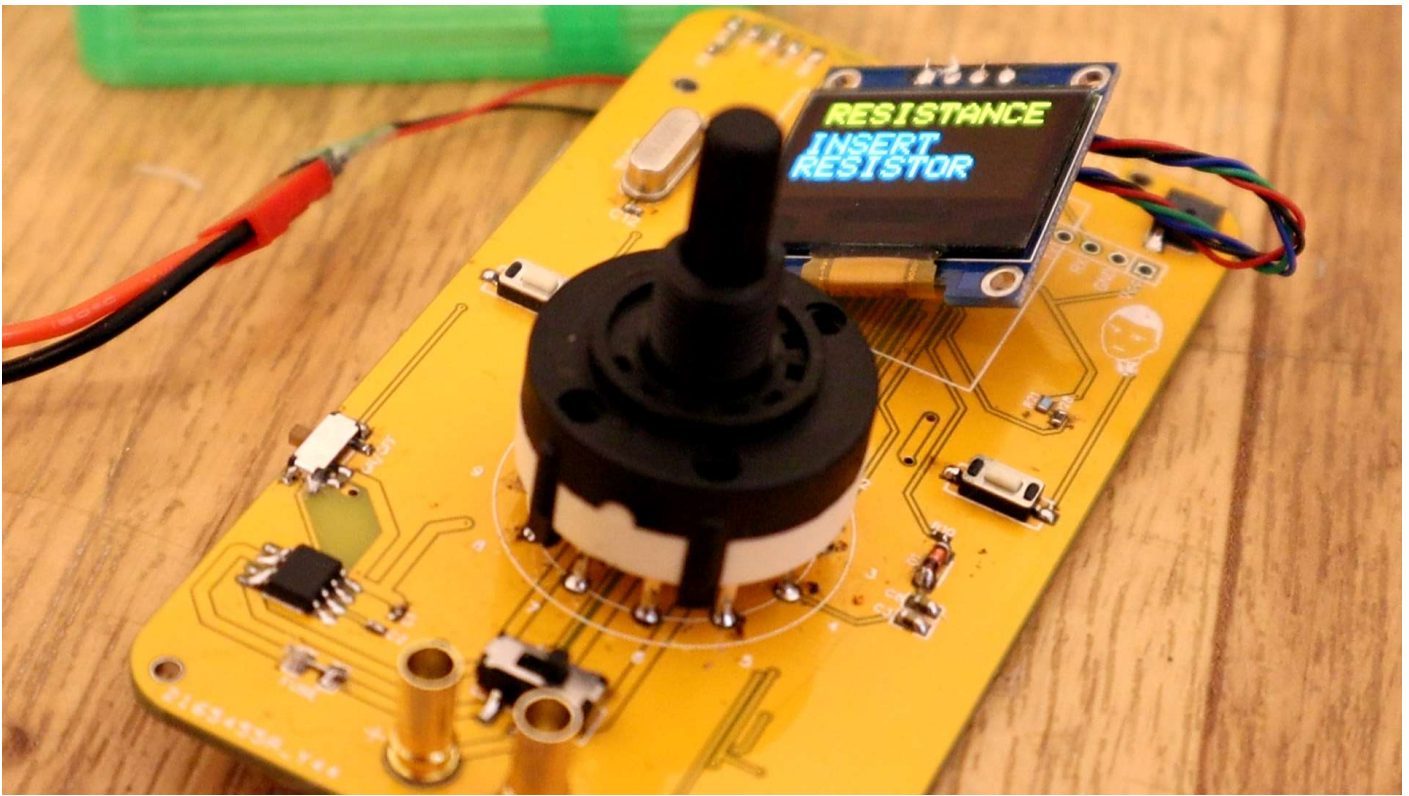

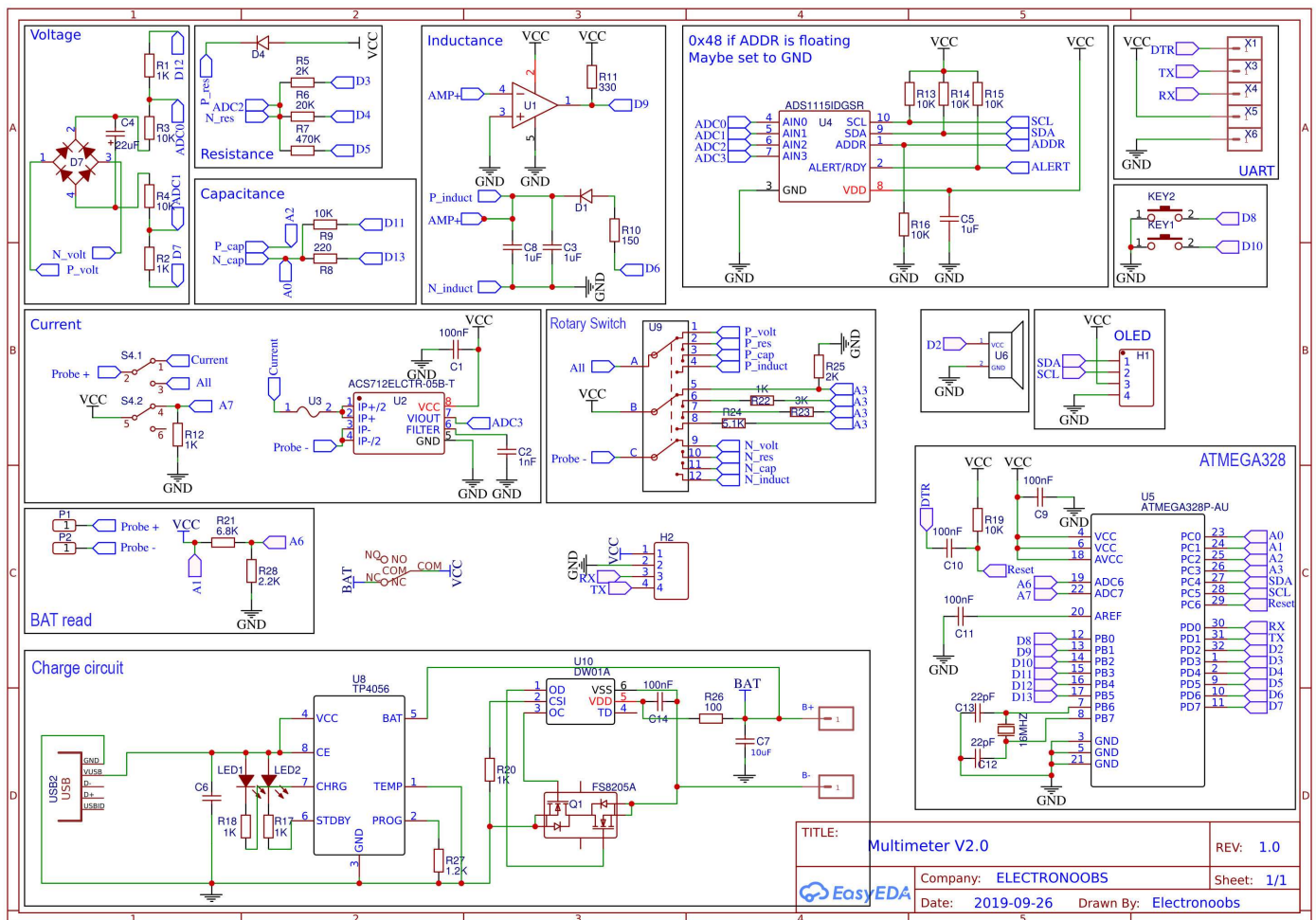PART 2 - Schematic


The schematic could be a bit tricky. But I've separated all parts. The first block should be the one in the middle which is the rotary switch. As you can see the input from the probe is divided into 4 outputs for voltage, resistance, capacitance and inductance. Current is done separately with a sliding switch (S4.1). The first measure block is the voltage one. As you can see we have the input from the probes connected to the full bridge rectifier and then we have a capacitor so we can store the voltage for AC mode. Then, that voltage is connected to some dividers and the output of the dividers to the ADC0 and ADC1 of the ADS1115, so in this way we can measure in differential mode and be able to measure negative voltages too.




(eng_arduino_tut112_sch1.php)


Next we have the blocks for resistance and capacitance. Resistance is easy. In the code, by changing D3, D4 and D5 to "LOW" we create a virtual GND to those pins. So, we can select from different voltage dividers in order to select scale. Then we measure the voltage with the ADC2 input of the ADS1115. We know the divider value and the measured voltage, so we can get the resistance value. Is that easy. You can see more about resistance measure here on this tutorial (https://www.electronoobs.com/eng_arduino_tut10.php).

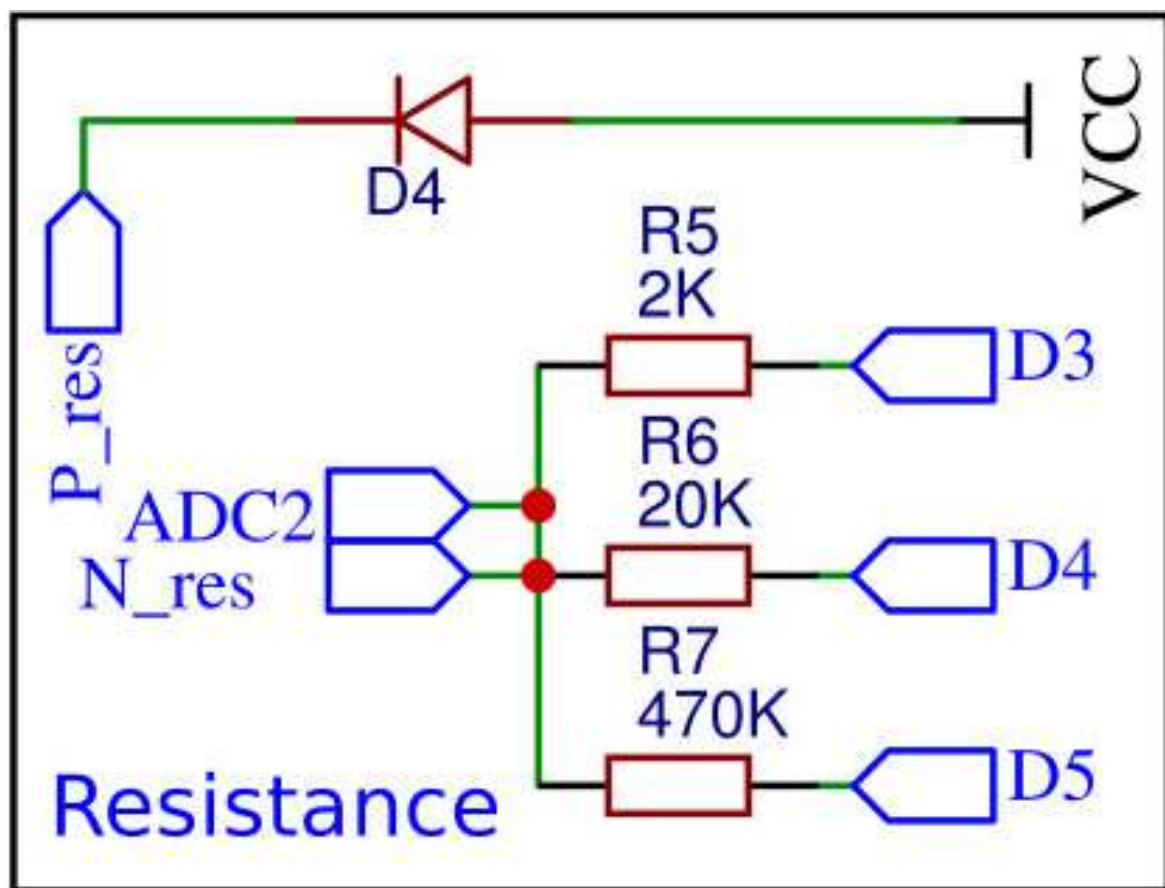Now for capacitance mode, we first charge up the capacitor with one of the D11 or D13 pins, depending on the mode. Then we measure the time it takes to discharge to 63.2% and then we use the time constant to get the capacitor value. See more on the tutorial here ([eng_arduino_tut10_1.php](https://www.electronoobs.com/eng_arduino_tut10_1.php)).



Capacitance

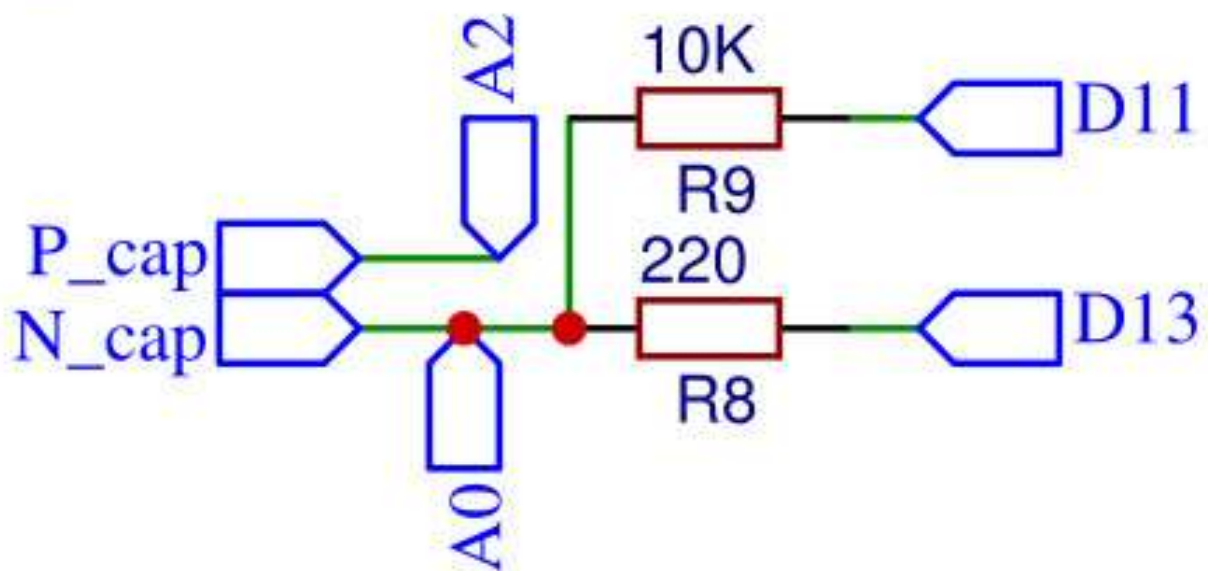


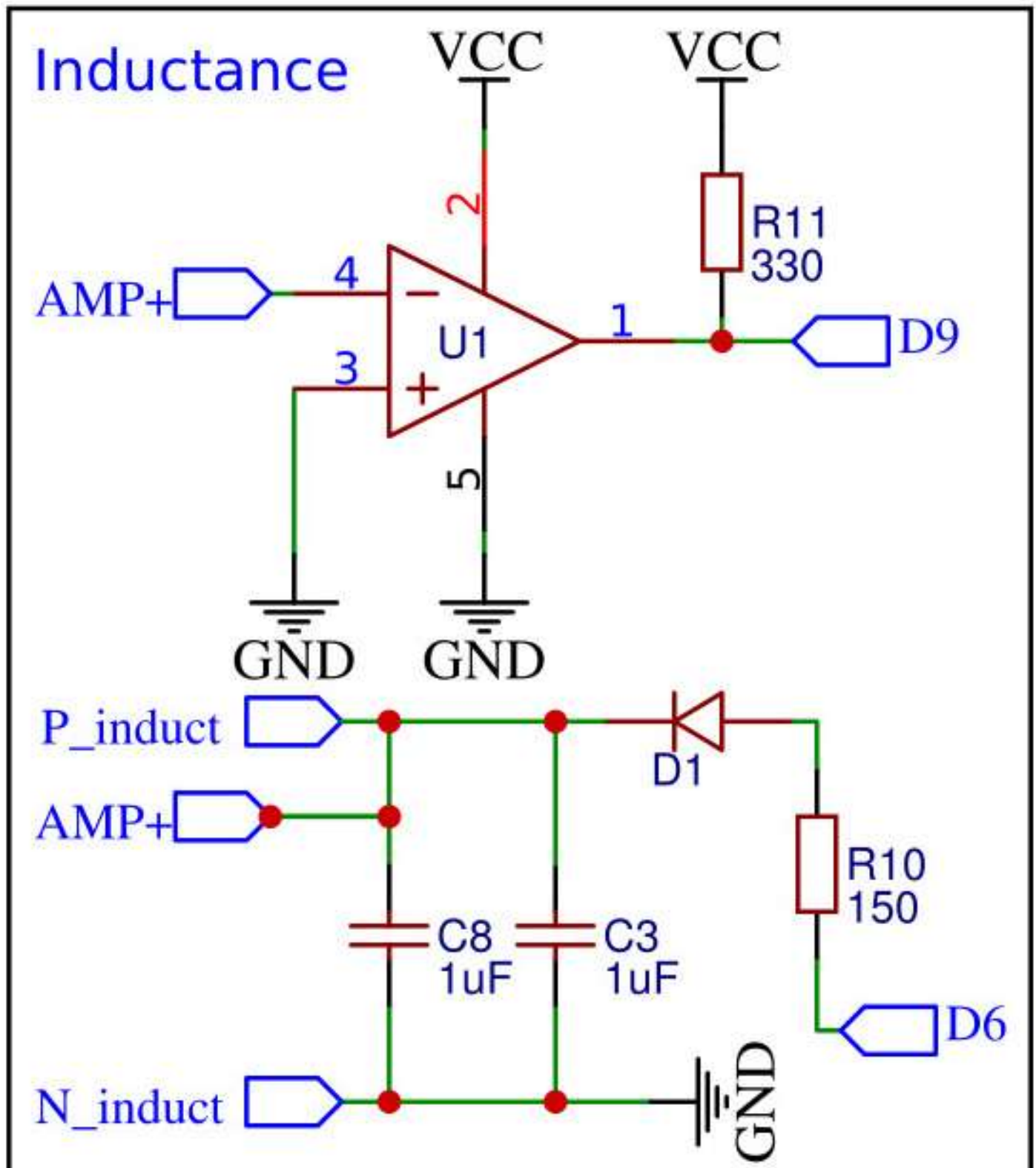

Next, we have inductance meter. here we have an "LC tank" made with those 1uF capacitors in parallel which make a 2uF cap, and the coil that we insert. An inductor in parallel with a capacitor is called an LC circuit, and it will electronically "ring" like a bell. Well regardless of the frequency or how hard a bell is struck, it will ring at it's resonating frequency. We will electronically strike the LC bell, wait a bit to let things resonate, then take a measurement.


So what we will do is applying a pulse signal to the LC circuit. In this case it will be 5 volts from the arduino from D6. We charge the circuit for some time. Then we change the voltage from 5 volts directly to 0. That pulse will make the circuit to resonate creating a cushioned sinusoidal signal oscilating at the resonant frequency. Using the OPAMP we pass that signal to square waves and then with the ARduino at pin D9 we measure the pulse lenght and bt taht we obtain the frequency. With the frequency, we get the inductor value because we already know the 2uF value of the capacitor. See more here (https://www.electrooobs.com/eng_arduino_tut10_3.php).

Current meter is simple. We connect the input to the ACS712 amplifier which is specially designed for current measure. It will give an analog output according to the current value and we know the gain. In this case I'm using the 20A model and the gain is 100mV/A output. So all we do in the code is to measure the analog output and then by knowing that each 100mV is 1A we can get the current value. You have some more theory here (https://www.electronoobs.com/eng_arduino_tut10_2.php).

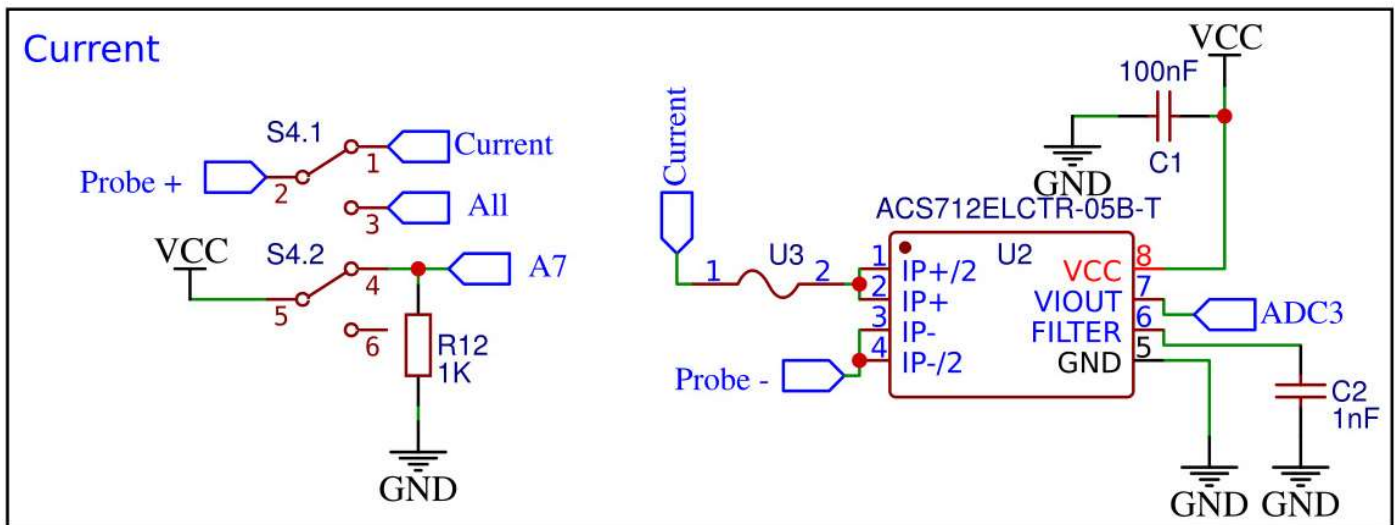

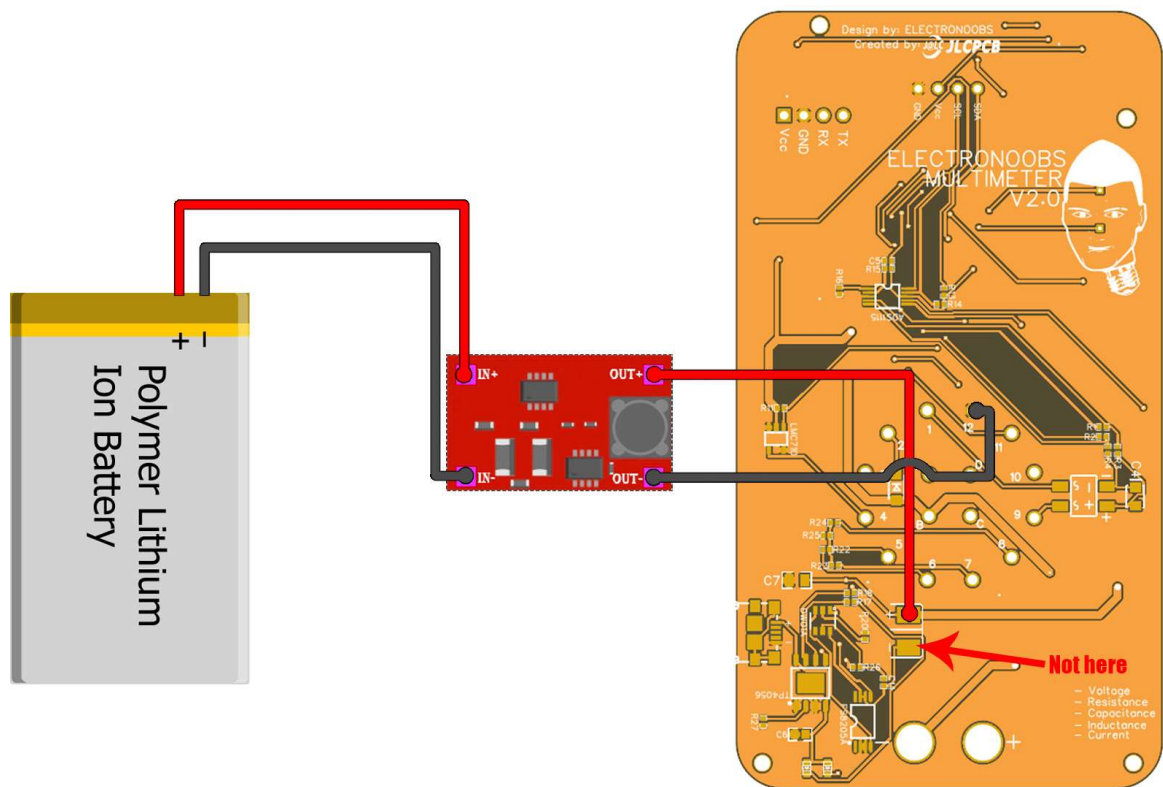PART 3 - Voltage problem

Once you see the PCB you will notice that on the back we have 2 pads for the battery (+ and -) and the charging circuit. We won't use these parts for now and this is why. In order to properly make calculations in the code, we also need to know the reference voltage of the battery. For that I've placed a divider on the schematic made with resistors R21 and R28. The input of that divider is the battery and using A6 we could measure the reference in the code using the internal reference of 1.1V. But, dumb as I am, if we set the analog reference to internal, then all analog measurements will be set to "INTERNAL" and we don't want that. So the solution is this:




Instead of measuring the battery value, what I've done is place a boost converter at the input that will always supply 5V. So now we know that the input will ALWAYS be 5V. But with this configuration we can't use the battery charger circuit. So, stay tuned for a future update of the circuit and PCB. So get the boost converter and set it to exactly 5V and then connect it to the PCB like shown above. One pin to the + pad and the other to GND of the PCB, **NOT to the "-" pad! So don't solder any components from the "Charge circuit" block from the schematic.**

PART 4 - Mount it all

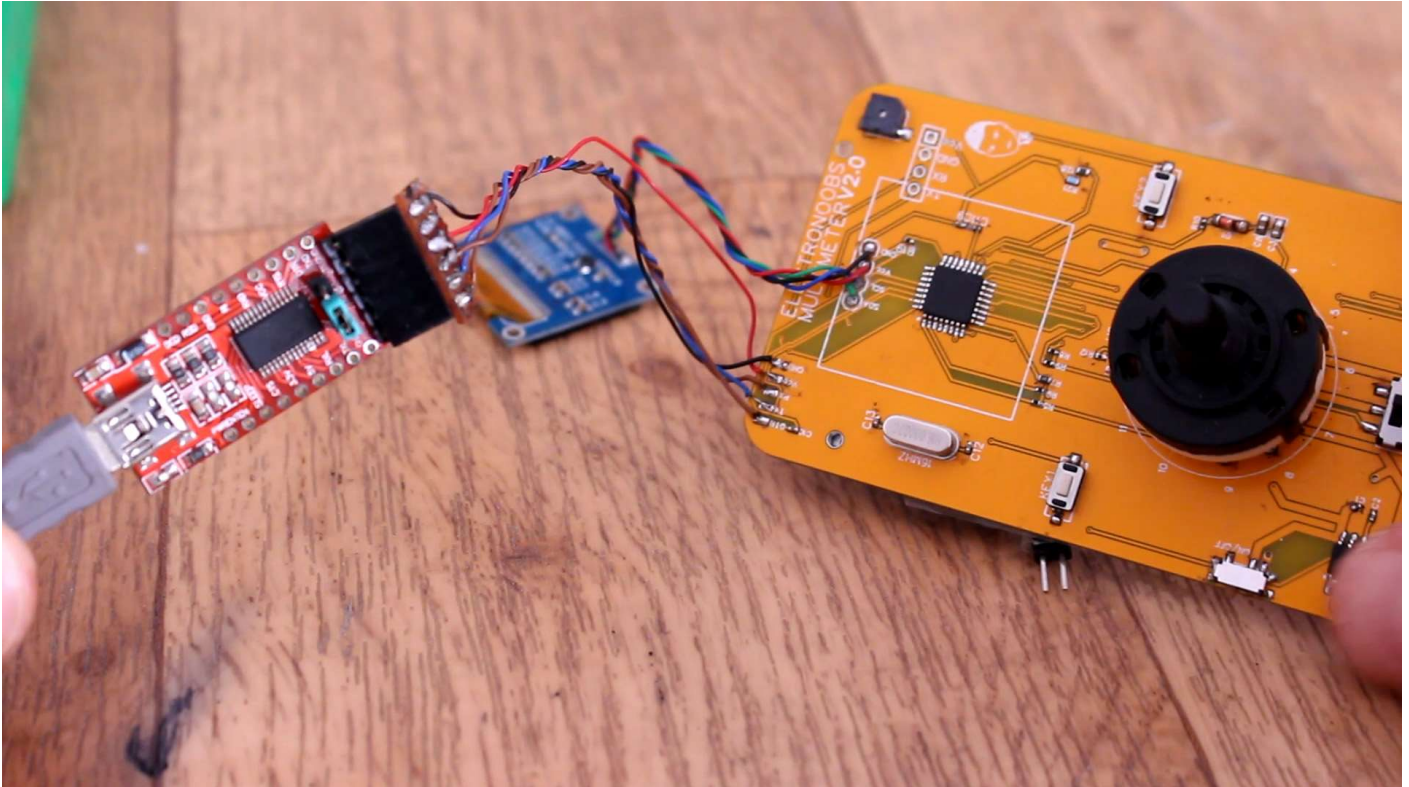4.1 The ATMEGA328 IC


Ok, get the GERBER files from below and order the PCB, or mount the same circuit on a prototyping PCB if you want. Anyway, get the PCB and let's start soldering components. **But that must go in this order.** First, we have to solder the ATMEGA328 and the basic components. That means all the components in the "ATMEGA328" block from the schematic. The chip, the crystal, the pullup R19, the small 22pF capacitors for the crystal and the DRT C10 capacitor of 100nF. Also solder C9 and C1 of 100nF as well. With these components the IC should work. To test if it does, connect the FTDI programmer to the UART pins, DTR to DTR, RX to TX, TX to RX, GND and Vcc and upload a code. For example upload a simple counter and print that on the monitor. If you get results, then the IC is working.

Download GERBER files [Download](#) (eng_arduino_tut112_gerber1.php)



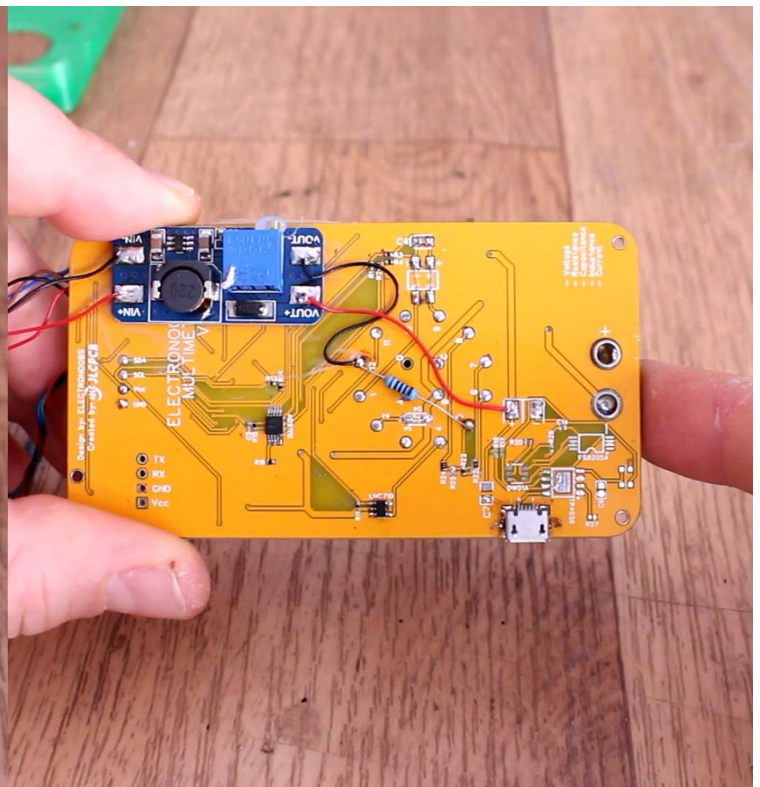4.2 The rest

If the IC works, you can now solder all the other components from the schematic. Use a lot of flux and food solder because the 0402 pads are very small. Or, if you want go here (<https://easyeda.com/Electronoobs/multimeter-v2-0>) to easyEDA and get the schematic and make your own board with bigger components. Connect the OLED display with thin wires. Connect and glue the battery and the boost converter on the back. Add the 4mm bullet connectors as probe input. **Check the rotary switch pins.** The switch has 3 inputs and 12 outputs. The PCB has 4 inputs. You must use inputs A, B and C. D is not used. Also, make sure which is output "1" of the rotary switch and make sure it will be connected to hole 1 on the PCB. Is time for the code.



For the code see next part...

[⬅️PREVIOUS TUTORIAL \(eng_arduino_tut111.php\)](#)

[NEXT PART➡️ \(eng_arduino_tut112_2.php\)](#)

Help me by sharing this post

Share 172



(<https://www.youtube.com/watch?v=5LpT8dV0K38>) (<https://www.instagram.com/p/B06t5B0N0QBS/>) (<https://www.facebook.com/arduinoideas/posts/10156163051106105>) (<https://twitter.com/arduinoideas/status/10156163051106105>)

Arduino Multimeter

page 1/2

Arduino based multimeter | V R C L I



ADVERTISERS

PCBWay

First 10 PCBs for \$0 in 24 Hrs!

**YOUR: Trustable, Affordable, Speedy
One-Stop Solution for
(PCBs/3D Printing/CNC...)**

Order Now



(<https://www.pcbway.es/?from=electronoobs.com00>)



(https://s.click.aliexpress.com/e/_9jqPR0?bz=300*250)

Curso Arduino Nivel 1

con @ELECTRONOBS

CURSO ARDUINO

¡Apúntate Ahora!

Español

- PARA TODO EL MUNDO
- Clases Video HD
- Acceso ilimitado
- DIRECTO con el Profesor
- Cuestionarios

Clases Video HD
Todo, todo, respuestas
sin conocimiento Previo
Sin Material previo
Dudas en directo
Pregúntale al Profesor
Para todo el mundo
Apóntate AHORA!

(<https://bit.ly/2JY8icE>)



(https://s.click.aliexpress.com/e/_AF7EeE?bz=500*500)



(<https://bit.ly/2ZNWgqy>)

Brushed motors Arduino drone - Part2 - Prototype + NRF24 code



DIY Inverter tutorial - Arduino or 555



TUTORIALS

[Arduino \(eng_tutoriales_arduino.php\)](#)

[Circuits \(eng_tutoriales_circuitos.php\)](#)

[Robotics \(eng_tutoriales_robotica.php\)](#)

[Arduino Course \(https://electronoobs.io/shop/index.php/courses/curso-arduino-desde-cero-nivel-1\)](https://electronoobs.io/shop/index.php/courses/curso-arduino-desde-cero-nivel-1)

[Blogs \(blogs.php\)](#)

SUPPORT

[Terms and Conditions \(terms_and_conditions.php\)](#)

[Privacy Policy \(privacy_policy.php\)](#)

[Contact me \(eng_contacto_mobile.php\)](#)

[Forum \(https://electronoobs.io/forum\)](https://electronoobs.io/forum)

ADVERTISERS

[Donate \(eng_donate.php\)](#)

[Reviews \(eng_reviews.php\)](#)

[Advertising \(eng_advertising.php\)](#)

ELECTRONOOPS Copyright ©2023, All rights reserved | [Terms and Conditions \(terms_and_conditions.php\)](#) | [Privacy Policy \(privacy_policy\)](#)